

# Chapter 23: Series and Parallel Circuits

## Practice Problems

page 471

1. There are three  $20\text{-}\Omega$  resistors connected in series across a  $120\text{-V}$  generator.

- a. What is the effective resistance of the circuit?

$$\begin{aligned} R &= R_1 + R_2 + R_3 \\ &= 20\ \Omega + 20\ \Omega + 20\ \Omega \\ &= 60\ \Omega \end{aligned}$$

- b. What is the current in the circuit?

$$I = V/R = (120\ \text{V})/(60\ \Omega) = 2.0\ \text{A}$$

2. A  $10\text{-}\Omega$  resistor, a  $15\text{-}\Omega$  resistor, and a  $5\text{-}\Omega$  resistor are connected in series across a  $90\text{-V}$  battery.

- a. What is the effective resistance of the circuit?

$$R = 10\ \Omega + 15\ \Omega + 5\ \Omega = 30\ \Omega$$

- b. What is the current in the circuit?

$$I = V/R = (90\ \text{V})/(30\ \Omega) = 3.0\ \text{A}$$

page 472

3. Consider a  $9\text{-V}$  battery in a circuit with three resistors connected in series.

- a. If the resistance of one of the devices increases, how will the series resistance change?

It will increase.

- b. What will happen to the current?

$I = V/R$ , so it will decrease.

- c. Will there be any change in the battery voltage?

No. It does not depend on the resistance.

## Practice Problems

4. Ten Christmas tree bulbs connected in series have equal resistances. When connected to  $120\text{-V}$  outlet, the current through the bulbs is  $0.06\ \text{A}$ .

- a. What is the effective resistance of the circuit?

$$R = V/I = (120\ \text{V})/(0.06\ \text{A}) = 2000\ \Omega$$

- b. What is the resistance of each bulb?

$$2000\ \Omega/10 = 200\ \Omega$$

page 474

5. A  $20.0\text{-}\Omega$  resistor and a  $30.0\text{-}\Omega$  resistor are connected in series and placed across a  $120\text{-V}$  potential difference.

- a. What is the effective resistance of the circuit?

$$R = 20.0\ \Omega + 30.0\ \Omega = 50.0\ \Omega$$

- b. What is the current in the circuit?

$$I = V/R = (120\ \text{V})/(50.0\ \Omega) = 2.40\ \text{A}$$

- c. What is the voltage drop across each resistor?

$$V = IR. \text{ Across } 20.0\ \Omega\text{-resistor,}$$

$$V = (2.40\ \text{A})(20.0\ \Omega) = 48.0\ \text{V.}$$

$$\text{Across } 30.0\ \Omega\text{-resistor,}$$

$$V = (2.40\ \text{A})(30.0\ \Omega) = 72.0\ \text{V}$$

- d. What is the voltage drop across the two resistors together?

$$V = 48.0\ \text{V} + 72.0\ \text{V} = 120\ \text{V}$$

6. Three resistors of  $3.0\ \text{k}\Omega$  ( $3.0 \times 10^3\ \Omega$ ),  $5.0\ \text{k}\Omega$ , and  $4.0\ \text{k}\Omega$  are connected in series across a  $12\text{-V}$  battery.

- a. What is the effective resistance?

$$R = 3.0\ \text{k}\Omega + 5.0\ \text{k}\Omega + 4.0\ \text{k}\Omega = 12.0\ \text{k}\Omega$$

## Practice Problems

- b. What is the current through the resistors?

$$I = V/R = (12 \text{ V})/(12.0 \text{ k}\Omega) \\ = 1.0 \text{ mA} = 1.0 \times 10^{-3} \text{ A}$$

- c. What is the voltage drop across each resistor?

$$V = IR, \\ \text{so } V = 3.0 \text{ V}, 5.0 \text{ V}, \text{ and } 4.0 \text{ V}$$

- d. Find the total voltage drop across the three resistors.

$$V = 3.0 \text{ V} + 5.0 \text{ V} + 4.0 \text{ V} \\ = 12.0 \text{ V}$$

7. A student makes a voltage divider from a 45-V battery, a 475-k $\Omega$  ( $475 \times 10^3 \Omega$ ) resistor, and a 235-k $\Omega$  resistor. The output voltage is measured across the smaller resistor. What is the voltage?

$$V_2 = VR_2/(R_1 + R_2) \\ = (45 \text{ V})(235 \text{ k}\Omega)/(475 \text{ k}\Omega + 235 \text{ k}\Omega) \\ = 15 \text{ V}$$

page 475

8. A photoresistor is used in a voltage divider as  $R_2$ .  $V = 9.0 \text{ V}$  and  $R_1 = 500 \Omega$ .

- a. What is the output voltage,  $V_2$  across  $R_2$ , when a bright light strikes the photoresistor and  $R_2 = 475 \Omega$ ?

$$V_2 = VR_2/(R_1 + R_2) \\ = (9.0 \text{ V})(475 \Omega)/(500 \Omega + 475 \Omega) \\ = 4.4 \text{ V}$$

- b. When the light is dim,  $R_2 = 4.0 \text{ k}\Omega$ . What is  $V_2$ ?

$$V_2 = VR_2/(R_1 + R_2) \\ = (9.0 \text{ V})(4.0 \text{ k}\Omega)/(0.50 \text{ k}\Omega + 4.0 \text{ k}\Omega) \\ = 8.0 \text{ V}$$

- c. When the photoresistor is in total darkness,  $R_2 = 0.40 \text{ M}\Omega$  ( $0.40 \times 10^6 \Omega$ ). What is  $V_2$ ?

$$V_2 = VR_2/(R_1 + R_2) \\ = \frac{(9.0 \text{ V})(4.0 \times 10^5 \Omega)}{(0.005 \times 10^5 \Omega + 4.0 \times 10^5 \Omega)} \\ = 9.0 \text{ V}$$

## Practice Problems

page 477

9. Three 15- $\Omega$  resistors are connected in parallel and placed across a 30-V potential difference.

- a. What is the equivalent resistance of the parallel circuit?

$$1/R = 1/R_1 + 1/R_2 + 1/R_3 \\ = 3/15 \Omega, R = 5.0 \Omega$$

- b. What is the current through the entire circuit?

$$I = V/R = (30 \text{ V})/(5.0 \Omega) = 6.0 \text{ A}$$

- c. What is the current through each branch of the parallel circuit?

$$I = V/R = (30 \text{ V})/(15.0 \Omega) = 2.0 \text{ A}$$

10. A 12.0- $\Omega$  resistor and a 15.0- $\Omega$  resistor are connected in parallel and placed across the terminals of a 15.0-V battery.

- a. What is the equivalent resistance of the parallel circuit?

$$1/R = 1/15.0 \Omega + 1/12.0 \Omega, \text{ so} \\ R = 6.67 \Omega$$

- b. What is the current through the entire circuit?

$$I = V/R = (15.0 \text{ V})/(6.67 \Omega) = 2.25 \text{ A}$$

- c. What is the current through each branch of the parallel circuit?

$$I = V/R = (15.0 \text{ V})/(15.0 \Omega) \\ = 1.00 \text{ A}, (15.0 \text{ V})/(12.0 \Omega) \\ = 1.25 \text{ A}$$

page 478

11. A 120.0- $\Omega$  resistor, a 60.0- $\Omega$  resistor, and a 40.0- $\Omega$  resistor are connected in parallel and placed across a potential difference of 12.0 V.

- a. What is the equivalent resistance of the parallel circuit?

$$1/R = 1/120.0 \Omega + 1/60.0 \Omega + 1/40.0 \Omega, \\ R = 20.0 \Omega$$

## Practice Problems

- b. What is the current through the entire circuit?

$$\begin{aligned} I &= V/R \\ &= (12.0 \text{ V})/(20.0 \Omega) \\ &= 0.600 \text{ A} \end{aligned}$$

- c. What is the current through each branch of the parallel circuit?

$$\begin{aligned} I &= V/R = (12.0 \text{ V})/(120.0 \Omega) \\ &= 0.100 \text{ A}, (12.0 \text{ V})/(60.0 \Omega) \\ &= 0.200 \text{ A}, (12.0 \text{ V})/(40.0 \Omega) \\ &= 0.300 \text{ A} \end{aligned}$$

12. Suppose the 12.0- $\Omega$  resistor in Practice Problem 10 is replaced by a 10.0- $\Omega$  resistor.

- a. Does the equivalent resistance become smaller, larger, or remain the same?

Smaller.

- b. Does the amount of current through the entire circuit change? in what way?

Gets larger.


- c. Does the amount of current through the 15.0- $\Omega$  resistor change? in what way?

No. It remains the same. Currents are independent.

page 484

13. Two 60- $\Omega$  resistors are connected in parallel. This parallel arrangement is connected in series with a 30- $\Omega$  resistor. The combination is then placed across a 120-V potential difference.

- a. Draw a diagram of the circuit.

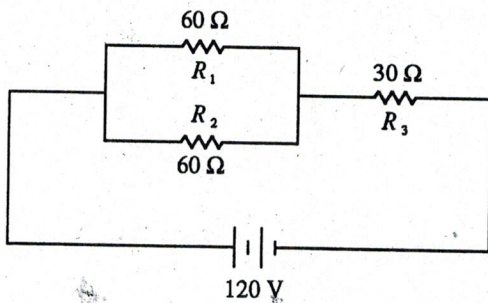

## Practice Problems

- b. What is the equivalent resistance of the parallel portion of the circuit?

$$\begin{aligned} \frac{1}{R} &= \frac{1}{60 \Omega} + \frac{1}{60 \Omega} = \frac{2}{60 \Omega} \\ R &= \frac{60 \Omega}{2} = 30 \Omega \end{aligned}$$

- c. What single resistance could replace the three original resistors?

$$R_{\text{eff}} = 30 \Omega + 30 \Omega = 60 \Omega$$

- d. What is the current in the circuit?

$$I = \frac{V}{R} = \frac{120 \text{ V}}{60 \Omega} = 2.0 \text{ A}$$

- e. What is the voltage drop across the 30- $\Omega$  resistor?

$$V_3 = IR_3 = (2.0)(30 \Omega) = 60 \text{ V}$$

- f. What is the voltage drop across the parallel portion of the circuit?


$$V = IR = (2.0 \text{ A})(30 \Omega) = 60 \text{ V}$$

- g. What is the current in each branch of the parallel portion of the circuit?

$$I = \frac{V}{R_1} = \frac{V}{R_2} = \frac{60 \text{ V}}{60 \Omega} = 1.0 \text{ A}$$

14. Three 15- $\Omega$  resistors are connected in parallel. This arrangement is connected in series with a 10- $\Omega$  resistor. The entire combination is then placed across a 45-V difference in potential.

- a. Draw a diagram of the circuit.

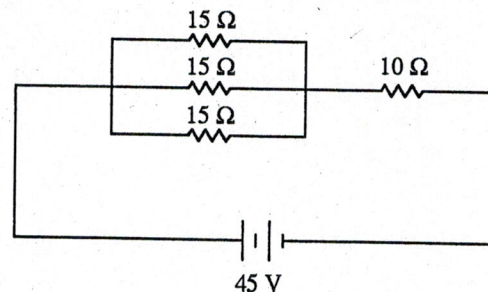

## Practice Problems

- b. What is the equivalent resistance of the parallel portion of the circuit?

$$\frac{1}{R} = \frac{1}{15 \Omega} + \frac{1}{15 \Omega} + \frac{1}{15 \Omega} = \frac{3}{15 \Omega}$$

$$R = \frac{15 \Omega}{3} = 5.0 \Omega$$

- c. What is the equivalent resistance of the entire circuit?

$$R_{\text{eff}} = 5 \Omega + 10 \Omega = 15 \Omega$$

- d. What is the current in the entire circuit?

$$I = \frac{V}{R_{\text{eff}}} = \frac{45 \text{ V}}{15 \Omega} = 3.0 \text{ A}$$

- e. What is the voltage drop across the 10- $\Omega$  resistor?

$$V = IR = (3.0 \text{ A})(10 \Omega) = 30 \text{ V}$$

15. Suppose you are given three 68- $\Omega$  resistors. You can use them in a series, parallel, or series-parallel circuit. Find the three different resistances you can produce in the circuit.

$$\text{Series: } 68 \Omega + 68 \Omega + 68 \Omega = 204 \Omega,$$

$$\text{Parallel: } 68 \Omega / 3 = 23 \Omega,$$

$$\text{Series Parallel: } 68 \Omega + 68 \Omega / 2 = 102 \Omega$$

---

## Chapter Review Problems

page 488–489

1. A 20.0- $\Omega$  lamp and a 5.0- $\Omega$  lamp are connected in series and placed across a difference in potential of 50 V.

- a. What is the effective resistance of the circuit?

$$20.0 \Omega + 5.0 \Omega = 25.0 \Omega$$

- b. What is the current in the circuit?

$$I = \frac{V}{R} = \frac{50 \text{ V}}{25.0 \Omega} = 2.0 \text{ A}$$

## Chapter Review Problems

- c. What is the voltage drop across each lamp?

$$V = IR = (2.0 \text{ A})(20.0 \Omega) = 40 \text{ V}$$

$$V = IR = (2.0 \text{ A})(5.0 \Omega) = 10 \text{ V}$$

- d. What is the power dissipated in each lamp?

$$P = IV = (2.0 \text{ A})(40 \text{ V}) = 80 \text{ W}$$

$$P = IV = (2.0 \text{ A})(10 \text{ V}) = 20 \text{ W}$$

2. Three identical lamps are connected in series to a 6.0-V battery. What is the voltage drop across each lamp?

Since each lamp is identical to the others, they will each have the same voltage drop of

$$\frac{6.0 \text{ V}}{3} = 2.0 \text{ V}.$$

3. The load across a 12-V battery consists of a series combination of three resistors of 15  $\Omega$ , 21  $\Omega$ , and 24  $\Omega$ .

- a. What is the total resistance of the load?

$$R = R_1 + R_2 + R_3 = 15 \Omega + 21 \Omega + 24 \Omega = 60 \Omega$$

- b. What is the current in the circuit?

$$I = \frac{V}{R} = \frac{12 \text{ V}}{60 \Omega} = 0.20 \text{ A}$$

4. The load across a battery consists of two resistors connected in series with values of 15  $\Omega$  and 45  $\Omega$ .

- a. What is the total resistance of the load?

$$R = R_1 + R_2 = 15 \Omega + 45 \Omega = 60 \Omega$$

- b. What is the voltage of the battery if the current in the circuit is 0.10 A?

$$V = IR = (60 \Omega)(0.10 \text{ A}) = 6.0 \text{ V}$$

5. A lamp having a resistance of 10  $\Omega$  is connected across a 15-V battery.

- a. What is the current through the lamp?

$$V = IR, \text{ so } I = \frac{V}{R} = \frac{15 \text{ V}}{10 \Omega} = 1.5 \text{ A}$$

- b. What resistance must be connected in series with the lamp to reduce the current to 0.50 A?

The total resistance is given by  $V = IR$ , so

$$R = \frac{V}{I} = \frac{15 \text{ V}}{0.50 \text{ A}} = 30 \Omega$$

And  $R = R_1 + R_2$ , so

$$R_2 = R - R_1 = 30 \Omega - 10 \Omega = 20 \Omega$$

6. A string of eighteen identical Christmas tree lights are connected in series to a 120-V source. The string dissipates 64 W.

- a. What is the equivalent resistance of the light string?

$$P = IV, \text{ so } I = \frac{P}{V} = \frac{64 \text{ W}}{120 \text{ V}} = 0.53 \text{ A and}$$

$$V = IR, \text{ so } R = \frac{V}{I} = \frac{120 \text{ V}}{0.53 \text{ A}} = 2.3 \times 10^2 \Omega$$

- b. What is the resistance of a single light?

$R$  is sum of resistances of 18 lamps, so each resistance is  $(230 \Omega)/18 = 13 \Omega$ .

- c. What power is dissipated by each lamp?

$$(64 \text{ W})/18 = 3.6 \text{ W}$$

7. One of the bulbs in the previous problem burns out. The lamp has a wire that shorts out the lamp filament when it burns out. This drops the resistance of the lamp to zero.

- a. What is the resistance of the light string now?

There are now 17 lamps in series instead of 18 lamps. The resistance is

$$\frac{17}{18}(2.3 \times 10^2 \Omega) = 2.2 \times 10^2 \Omega$$

- b. Find the power dissipated by the string.

$$I = \frac{V}{R} = \frac{120 \text{ V}}{2.2 \times 10^2 \Omega} = 0.55 \text{ A and}$$

$$P = IV = (0.55 \text{ A})(120 \text{ V}) = 66 \text{ W}$$

- c. Did the power go up or down when a bulb burned out?

It increased!

8. A 75.0-W bulb is connected to a 120-V source.

- a. What is the current through the bulb?

$$P = IV, \text{ so } I = \frac{P}{V} = \frac{75.0 \text{ W}}{120 \text{ V}} = 0.625 \text{ A}$$

- b. What is the resistance of the bulb?

$$V = IR, \text{ so } R = \frac{V}{I} = \frac{120 \text{ V}}{0.625 \text{ A}} = 192 \Omega$$

- c. A lamp dimmer puts a resistance in series with the bulb. What resistance would be needed to reduce the current to 0.300 A?

$$V = IR, \text{ so } R = \frac{V}{I} = \frac{120 \text{ V}}{0.300 \text{ A}} = 400 \Omega \text{ and}$$

$$R = R_1 + R_2, \text{ so}$$

$$R_2 = R - R_1 = 400 \Omega - 192 \Omega = 208 \Omega$$

9. In the previous problem, you found the resistance of a lamp and a dimmer resistor.

- a. Assuming the resistances are constant, find the voltage drops across the lamp and the resistor.

$$V = IR = (0.300 \text{ A})(192 \Omega) = 57.6 \text{ V}$$

$$V = IR = (0.300 \text{ A})(208 \Omega) = 62.4 \text{ V}$$

- b. Find the power dissipated by the lamp.

$$P = IV = (0.300 \text{ A})(57.6 \text{ V}) = 17.3 \text{ W}$$

- c. Find the power dissipated by the dimmer resistor.

$$P = IV = (0.300 \text{ A})(62.4 \text{ V}) = 18.7 \text{ W}$$

10. Amy needs 5.0 V for some integrated circuit experiments. She uses a 6.0-V battery and two resistors to make a voltage divider. One resistor is 330  $\Omega$ . She decides to make the other resistor smaller. What value should it have?

$V_2 = \frac{VR_2}{R_1 + R_2}$ . Since  $V_2$  is more than half  $V$ , the voltage across  $R_2$  is larger than that across  $R_1$ , so  $R_2 > R_1$ .

$$R_1 = \frac{VR_2}{V_2} - R_2 = \frac{(6.0 \text{ V})(330 \Omega)}{5.0 \text{ V}} - 330 \Omega = 66 \Omega$$

11. Pete is designing a voltage divider using a 12.0-V battery and a 100- $\Omega$  resistor as  $R_2$ . What resistor should be used as  $R_1$  if the output voltage across  $R_2$  is to be 4.00 V?

$$V_2 = \frac{VR_2}{R_1 + R_2}, \text{ or } R_1 + R_2 = \frac{VR_2}{R_2}, \text{ so}$$

$$R_1 = \frac{VR_2}{V_2} - R_2 = \frac{(12.0 \text{ V})(100 \Omega)}{4.00 \text{ V}} - 100 \Omega \\ = 200 \Omega$$

12. A typical television dissipates 275 W when connected to a 120-V outlet.

- a. Find the resistance of the television.

$$P = IV \text{ and } I = \frac{V}{R}, \text{ so } P = \frac{V^2}{R}, \text{ or}$$

$$R = \frac{V^2}{P} = \frac{(120 \text{ V})^2}{275 \text{ W}} = 52.4 \Omega$$

- b. The television and connecting wires, with a resistance of 2.5  $\Omega$ , form a series circuit that works like a voltage divider. Find the voltage drop across the television.

$$V_1 = \frac{VR_1}{R_1 + R_2} = \frac{(120 \text{ V})(52.4 \Omega)}{52.4 \Omega + 2.5 \Omega} \\ = 115 \text{ V}$$

- c. A 12- $\Omega$  hair dryer is now plugged into the same outlet. Find the equivalent resistance of the two appliances.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{52.4 \Omega} + \frac{1}{12 \Omega} = 9.8 \Omega$$

- d. Find the voltage drop across the television and hair dryer combination. The lower voltage explains why the television picture sometimes shrinks when another appliance is turned on.

$$V_1 = \frac{VR_1}{R_1 + R_2} = \frac{(120 \text{ V})(9.8 \Omega)}{9.8 \Omega + 2.5 \Omega} = 96 \text{ V}$$

13. Three identical lamps are connected in parallel to each other and then connected to a 6.0-V battery. What is the voltage drop across each lamp?

In parallel circuits, the voltage drop across each branch are the same, in this case 6.0 V.

14. A 16.0- $\Omega$  and a 20.0- $\Omega$  resistor are connected in parallel. A difference in potential of 40.0 V is applied to the combination.

- a. Compute the equivalent resistance of the parallel circuit.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{16.0 \Omega} + \frac{1}{20.0 \Omega}$$

$$R = \frac{1}{0.1125 \Omega} = 8.89 \Omega$$

- b. What is the current in the circuit?


$$I = \frac{V}{R} = \frac{40.0 \text{ V}}{8.89 \Omega} = 4.50 \text{ A}$$

- c. How large is the current through the 16.0- $\Omega$  resistor?

$$I_1 = \frac{V}{R_1} = \frac{40.0 \text{ V}}{16.0 \Omega} = 2.50 \text{ A}$$

15. During a laboratory exercise, you are supplied with the following apparatus: a battery of potential difference  $V$ , two heating elements of low resistance that can be placed in water, an ammeter of negligible resistance, a voltmeter of extremely high resistance, wires of negligible resistance, a beaker that is well-insulated and has negligible heat capacity, 100.0 g of water at 25°C.

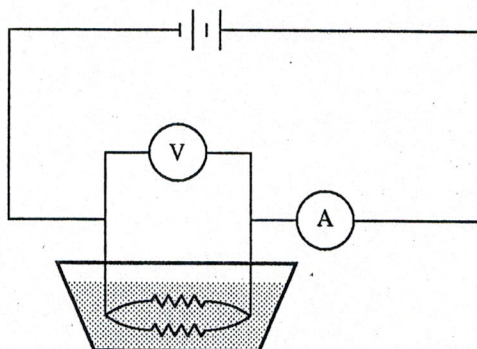- a. By means of a diagram using standard symbols, show how these components should be connected to heat the water as rapidly as possible.



- b. If the voltmeter reading holds steady at 50.0 V and the ammeter reading holds steady at 5.0 A, estimate the time in seconds required to completely vaporize the water in the beaker. Use  $4200 \text{ J/kg} \cdot \text{C}^\circ$  as the specific heat of water and  $2.30 \times 10^6 \text{ J/kg}$  as the heat of vaporization of water.

$$\Delta Q = mc\Delta T = (100.0 \text{ g})(4.2 \text{ J/g} \cdot \text{C}^\circ)(75 \text{ C}^\circ) = 32\,000 \text{ J}$$

$$\Delta Q = mL_v = (100.0 \text{ g})(2300 \text{ J/g}) = 230\,000 \text{ J}$$

$$\Delta Q_{\text{total}} = 32\,000 \text{ J} + 230\,000 \text{ J} = 260\,000 \text{ J}$$

Energy is provided at the rate of

$$P = IV = (5.0 \text{ A})(50.0 \text{ V}) = 250 \text{ J/s}$$

The time required is  $t = \frac{260\,000 \text{ J}}{250 \text{ J/s}} = 1.0 \times 10^3 \text{ s}$

16. A circuit contains six  $240\text{-}\Omega$  lamps,  $60\text{-W}$  bulbs, and a  $10.0\text{-}\Omega$  heater connected in parallel. The voltage across the circuit is 120 V. What is the current in the circuit

- a. when four lamps are turned on?

$$\begin{aligned} \frac{1}{R} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \\ &= \frac{1}{240 \Omega} + \frac{1}{240 \Omega} + \frac{1}{240 \Omega} + \frac{1}{240 \Omega} \\ &= \frac{4}{240 \Omega}, \text{ so} \end{aligned}$$

$$R = \frac{240 \Omega}{4} = 60 \Omega$$

$$I = \frac{V}{R} = \frac{120 \text{ V}}{60 \Omega} = 2.0 \text{ A}$$

- b. when all six lamps are turned on?

$$\frac{1}{R} = \frac{6}{240 \Omega}$$

$$R = \frac{240 \Omega}{6} = 40 \Omega$$

$$I = \frac{V}{R} = \frac{120 \text{ V}}{40 \Omega} = 3.0 \text{ A}$$

- c. if all six lamps and the heater are operating?

$$\frac{1}{R} = \frac{1}{40 \Omega} + \frac{1}{10.0 \Omega} = \frac{5}{40 \Omega}$$


$$R = \frac{40 \Omega}{5} = 8.0 \Omega$$

$$I = \frac{V}{R} = \frac{120 \text{ V}}{8.0 \Omega} = 15 \text{ A}$$

- d. If the circuit has a fuse rated at 12 A, will it melt if everything is on?

Yes. The 15-A current will melt the 12-A fuse.

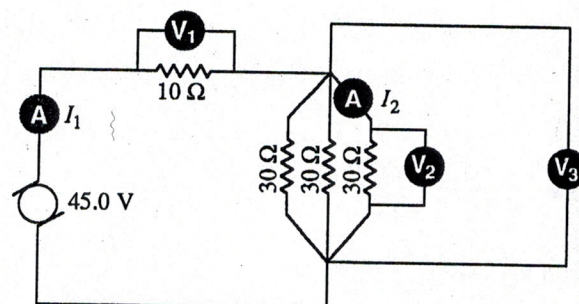17. Determine the reading of each ammeter and each voltmeter in Figure 23-18.



The three resistors in parallel have a total resistance of

$$\begin{aligned} \frac{1}{R_B} &= \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \\ &= \frac{1}{30.0 \Omega} + \frac{1}{30.0 \Omega} + \frac{1}{30.0 \Omega}, \text{ so} \end{aligned}$$

$$R_B = 10.0 \Omega.$$

The total resistance of the circuit is

$$R_T = R_1 + R_B = 10.0 \Omega + 10.0 \Omega = 20.0 \Omega$$

$$I_1 = \frac{V}{R_T} = \frac{45.0 \text{ V}}{20.0 \Omega} = 2.25 \text{ A}$$

$$V_1 = IR_1 = (2.25 \text{ A})(10.0 \Omega) = 22.5 \text{ V}$$

Because the ammeter has an internal resistance of almost zero,

$$V_2 = V_3 = 45.0 \text{ V} - V_1 = 45.0 \text{ V} - 22.5 \text{ V} = 22.5 \text{ V}$$

$$I_2 = \frac{V_2}{R_2} = \frac{22.5 \text{ V}}{30.0 \Omega} = 0.750 \text{ A}$$

18. Determine the power used by each resistance shown in Figure 23-18.

Some information is from the previous problem. See figure from Problem 17.


In the  $10\text{-}\Omega$  resistor,

$$P_1 = I_1 V_1 = (2.25 \text{ A})(22.5 \text{ V}) = 50.6 \text{ W}$$

In each of the  $30\text{-}\Omega$  resistors the power will be equal to

$$P = IV = (0.750 \text{ A})(22.5 \text{ V}) = 16.9 \text{ W.}$$

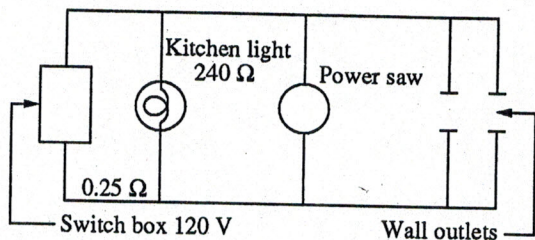19. A typical home circuit is diagrammed in Figure 23-19. Note that the lead lines to the kitchen lamp each have very low resistances of  $0.25 \text{ }\Omega$ . The lamp has a resistance of  $240.0 \text{ }\Omega$ . Although the circuit is a parallel circuit, the lead lines are in series with each of the components of the circuit.



- a. Compute the effective resistance of the circuit consisting of just the light and the lead lines to and from the light.

$$R = 0.25 \text{ }\Omega + 0.25 \text{ }\Omega + 240 \text{ }\Omega = 240 \text{ }\Omega$$

- b. Find the current to the bulb.

$$I = \frac{V}{R} = \frac{120 \text{ V}}{240 \text{ }\Omega} = 0.50 \text{ A}$$

- c. Find the power rating of the bulb.

$$P = IV = (0.50 \text{ A})(120 \text{ V}) = 60 \text{ W}$$

- d. Since the current in the bulb is  $0.50 \text{ A}$ , the current in the lead lines must also be  $0.50 \text{ A}$ . Calculate the voltage drop due to the two leads.

$$V = IR = (0.50 \text{ A})(0.50 \text{ }\Omega) = 0.25 \text{ V}$$

20. A power saw is operated by an electric motor. When the electric motor is first turned on, it has a very low resistance. Suppose that the kitchen light discussed in the previous problem is on and a power saw is suddenly turned on. The saw plus the lead lines have an initial total resistance of  $6.0 \text{ }\Omega$ .

- a. Compute the effective resistance of the light-saw parallel circuit.

$$\frac{1}{R} = \frac{1}{240 \text{ }\Omega} + \frac{1}{6.0 \text{ }\Omega}$$

$$R = 5.9 \text{ }\Omega$$

$$R_{\text{eff}} = 5.9 \text{ }\Omega + 0.25 \text{ }\Omega + 0.25 \text{ }\Omega = 6.4 \text{ }\Omega$$

- b. What current flows to the light?

$$I = \frac{V}{R} = \frac{120 \text{ V}}{6.4 \text{ }\Omega} = 19 \text{ A}$$

- c. What is the total voltage drop across the two leads to the light?

$$V = IR = (19 \text{ A})(0.50 \text{ }\Omega) = 9.5 \text{ V}$$

- d. What voltage remains to operate the light? Will this voltage cause the light to dim temporarily?

$$V = 120 \text{ V} - 9.5 \text{ V} = 110 \text{ V}$$

Yes, this will cause a momentary dimming.

### Supplementary Problems (Appendix B)

1. The load across a  $50.0\text{-V}$  battery consists of a series combination of two lamps with resistances of  $125 \text{ }\Omega$  and  $225 \text{ }\Omega$ .

- a. Find the total resistance of the circuit.

$$R_T = R_1 + R_2 = 125 \text{ }\Omega + 225 \text{ }\Omega = 350 \text{ }\Omega$$

- b. Find the current in the circuit.

$$V = IR, \text{ so } I = \frac{V}{R} = \frac{50.0 \text{ V}}{350 \text{ }\Omega} = 0.143 \text{ A}$$




- c. Find the potential difference across the 125- $\Omega$  lamp.

$$V = IR = (0.143 \text{ A})(125 \Omega) = 17.9 \text{ V}$$

2. The load across a 12-V battery consists of a series combination of three resistances that are 15  $\Omega$ , 21  $\Omega$ , and 24  $\Omega$  respectively.

- a. Draw the circuit diagram.

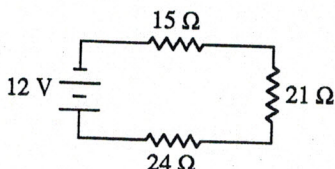

- b. What is the total resistance of the load?

$$R_T = R_1 + R_2 + R_3 = 15 \Omega + 21 \Omega + 24 \Omega = 60 \Omega$$

- c. What is the magnitude of the circuit current?

$$V = IR, \text{ so } I = \frac{V}{R} = \frac{12 \text{ V}}{60 \Omega} = 0.20 \text{ A}$$

3. The load across a 12-V battery consists of a series combination of three resistances  $R_1$ ,  $R_2$ , and  $R_3$ .  $R_1$  is 210  $\Omega$ ,  $R_2$  is 350  $\Omega$  and  $R_3$  is 120  $\Omega$ .

- a. Find the equivalent resistance of the circuit.

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 \\ &= 210 \Omega + 350 \Omega + 120 \Omega \\ &= 680 \Omega \end{aligned}$$

- b. Find the current in the circuit.

$$V = IR, \text{ so}$$

$$I = \frac{V}{R} = \frac{12 \text{ V}}{680 \Omega} = 1.8 \times 10^{-2} \text{ A} = 18 \text{ mA}$$

- c. Find the potential difference across  $R_3$ .

$$V = IR = (1.8 \times 10^{-2} \text{ A})(120 \Omega) = 2.2 \text{ V}$$

4. The load across a 40-V battery consists of a series combination of three resistances,  $R_1$ ,  $R_2$ , and  $R_3$ .  $R_1$  is 240  $\Omega$ , and  $R_3$  is 120  $\Omega$ . The potential difference across  $R_1$  is 24 V.

- a. Find the current in the circuit.

$$V = IR, \text{ so } I = \frac{V_1}{R_1} = \frac{24 \text{ V}}{240 \Omega} = 0.10 \text{ A}$$

- b. Find the equivalent resistance of the circuit.

$$V = IR, \text{ so } R = \frac{V}{I} = \frac{40 \text{ V}}{0.10 \text{ A}} = 400 \Omega$$

- c. Find the resistance of  $R_2$ .

$$R_T = R_1 + R_2 + R_3, \text{ so}$$

$$\begin{aligned} R_2 &= R_T - R_1 - R_3 \\ &= 400 \Omega - 240 \Omega - 120 \Omega \\ &= 40 \Omega \end{aligned}$$

5. Pete is designing a voltage divider using a 12.0-V battery and a 100- $\Omega$  resistor as  $R_2$ . What resistor should be used as  $R_1$  if the output voltage is 4.75 V?

$$V_2 = \frac{VR_2}{R_1 + R_2}, \text{ so } (R_1 + R_2)V_2 = VR_2 \text{ and}$$

$$R_1V_2 = VR_2 - V_2R_2, \text{ so}$$

$$\begin{aligned} R_1 &= \left[ \frac{V - V_2}{V_2} \right] R_2 = \left[ \frac{12.0 - 4.75}{4.75} \right] 100 \Omega \\ &= 153 \Omega \end{aligned}$$

6. Two resistances, one 12  $\Omega$  and the other 18  $\Omega$ , are connected in parallel. What is the equivalent resistance of the parallel combination?

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{12 \Omega} + \frac{1}{18 \Omega}, \text{ so } R = 7.2 \Omega$$

7. Three resistances of 12  $\Omega$  each are connected in parallel. What is the equivalent resistance?

$$\begin{aligned} \frac{1}{R} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{12 \Omega} + \frac{1}{12 \Omega} + \frac{1}{12 \Omega} \\ &= \frac{3}{12 \Omega} = \frac{1}{4.0 \Omega}, \text{ so } R = 4.0 \Omega \end{aligned}$$

8. Two resistances, one  $62\ \Omega$  and the other  $88\ \Omega$ , are connected in parallel. The resistors are then connected to a  $12\ \text{V}$  battery.

- a. What is the equivalent resistance of the parallel combination?

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{62\ \Omega} + \frac{1}{88\ \Omega}$$

$$\text{so } R = 36\ \Omega$$

- b. What is the current through each resistor?

$$V = IR, \text{ so } I = \frac{V}{R} = \frac{12\ \text{V}}{62\ \Omega} = 0.19\ \text{A}$$

$$I = \frac{V}{R} = \frac{12\ \text{V}}{88\ \Omega} = 0.14\ \text{A}$$

9. A  $35\ \Omega$ ,  $55\ \Omega$  and  $85\ \Omega$  resistor are connected in parallel. The resistors are then connected to a  $35\ \text{V}$  battery.

- a. What is the equivalent resistance of the parallel combination?

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{35\ \Omega} + \frac{1}{55\ \Omega} + \frac{1}{85\ \Omega}, \text{ so}$$

$$R = 17\ \Omega$$

- b. What is the current through each resistor?

$$V = IR, \text{ so } I_1 = \frac{V}{R_1} = \frac{35\ \text{V}}{35\ \Omega} = 1.0\ \text{A}$$

$$I_2 = \frac{V}{R_2} = \frac{35\ \text{V}}{55\ \Omega} = 0.64\ \text{A}$$

$$I_3 = \frac{V}{R_3} = \frac{35\ \text{V}}{85\ \Omega} = 0.41\ \text{A}$$

10. A  $110\ \text{V}$  household circuit that contains a  $1800\ \text{W}$  microwave, a  $1000\ \text{W}$  toaster, and a  $800\ \text{W}$  coffee maker is connected to a  $20\ \text{A}$  fuse. Will the fuse melt if the microwave and the coffee maker are both on?

$$P = IV, \text{ so}$$


$$I = \frac{P}{V} = \frac{1800\ \text{W}}{110\ \text{V}} = 16.4\ \text{A} \quad (\text{microwave})$$

$$I = \frac{P}{V} = \frac{800\ \text{W}}{110\ \text{V}} = 7.27\ \text{A} \quad (\text{coffee maker})$$

Total current of  $23.7\ \text{A}$  is greater than  $20\ \text{A}$  so the fuse will melt.

11. Resistors  $R_1$ ,  $R_2$ , and  $R_3$  have resistances of  $15.0\ \Omega$ ,  $9.0\ \Omega$ , and  $8.0\ \Omega$  respectively.  $R_1$  and  $R_2$  are connected in series and their combination is in parallel with  $R_3$  to form a load across a  $6.0\ \text{V}$  battery.

- a. Draw the circuit diagram.

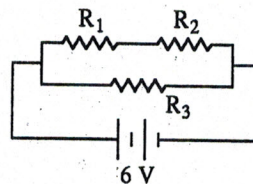

- b. What is the total resistance of the load?

$$R_1 + R_2 = 15.0\ \Omega + 9.0\ \Omega = 24.0\ \Omega$$

$$\frac{1}{R_T} = \frac{1}{R_{12}} + \frac{1}{R_3} = \frac{1}{24.0\ \Omega} + \frac{1}{8.0\ \Omega}, \text{ so}$$

$$R_T = 6.0\ \Omega$$

- c. What is the magnitude of the circuit current?

$$V = IR, \text{ so } I = \frac{V}{R} = \frac{6.0\ \text{V}}{6.0\ \Omega} = 1.0\ \text{A}$$

- d. What is the current in  $R_3$ ?

$$V = IR, \text{ so } I_3 = \frac{V}{R_3} = \frac{6.0\ \text{V}}{8.0\ \Omega} = 0.75\ \text{A}$$

- e. What is the potential difference across  $R_2$ ?

$$I_T = I_2 + I_3, \text{ so}$$


$$I_2 = I_T - I_3 = 1.0\ \text{A} - 0.75\ \text{A} = 0.25\ \text{A} \text{ and}$$

$$V_2 = I_2 R_2 = (0.25\ \text{A})(9.0\ \Omega) = 2.3\ \text{V}$$

## Supplemental Problems

12. A  $15.0\ \Omega$  resistor is connected in series to a 120 Volt generator and two  $10.0\ \Omega$  resistors that are connected in parallel to each other.

a. Draw the circuit diagram.

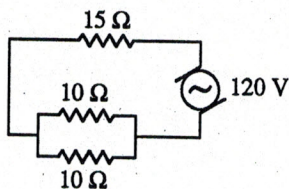

b. What is the total resistance of the load?

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{10.0\ \Omega} + \frac{1}{10.0\ \Omega} = \frac{1}{5.0\ \Omega}$$

$$\text{so } R_{12} = 5.0\ \Omega$$

$$R_T = R_3 + R_{12} = 15.0\ \Omega + 5.0\ \Omega = 20.0\ \Omega$$

c. What is the magnitude of the circuit current?

$$V = IR, \text{ so } I = \frac{V}{R} = \frac{120\ \text{V}}{20.0\ \Omega} = 6.00\ \text{A}$$

d. What is the current in one of the  $10.0\ \Omega$  resistors?

The current would divide equally, so 3.00 A.

e. What is the potential difference across  $15.0\ \Omega$  resistor?

$$V = IR = (6.00\ \text{A})(15.0\ \Omega) = 90.0\ \text{V}$$

13. How would you change the resistance of a voltmeter to allow the voltmeter to measure a larger potential difference?

Increase the resistance.

14. How would you change the shunt in an ammeter to allow the ammeter to measure a larger current?

Decrease the resistance of the shunt.

## Supplemental Problems

15. An ohmmeter is made by connecting a 6.0 V battery in series with an adjustable resistor and an ideal ammeter. The ammeter deflects full-scale with a current of 1.0 mA. The two leads are touched together and the resistance is adjusted so 1.0 mA current flows.

a. What is the resistance of the adjustable resistor?

$$V = IR, \text{ so}$$

$$R = \frac{V}{I} = \frac{6.0\ \text{V}}{1.0 \times 10^{-3}\ \text{A}} = 6.0 \times 10^3\ \Omega$$

b. The leads are now connected to an unknown resistance. What external resistance would produce a reading of 0.50 mA, half full-scale?

$$R = \frac{V}{I} = \frac{6.0\ \text{V}}{0.50 \times 10^{-3}\ \text{A}} = 1.2 \times 10^4\ \Omega \text{ and}$$

$$R_T = R_1 + R_e, \text{ so}$$

$$R_e = R_T - R_1 = 1.2 \times 10^4\ \Omega - 6.0 \times 10^3\ \Omega = 6 \times 10^3\ \Omega$$

c. What external resistance would produce a reading of 0.25 mA, quarter-scale?

$$R = \frac{V}{I} = \frac{6.0\ \text{V}}{0.25 \times 10^{-3}\ \text{A}} = 2.4 \times 10^4\ \Omega \text{ and}$$

$$R_e = R_T - R_1 = 2.4 \times 10^4\ \Omega - 6.0 \times 10^3\ \Omega = 1.8 \times 10^4\ \Omega$$

d. What external resistance would produce a reading of 0.75 mA, three-quarter full-scale?

$$R = \frac{V}{I} = \frac{6.0\ \text{V}}{0.75 \times 10^{-3}\ \text{A}} = 8.0 \times 10^3\ \Omega \text{ and}$$

$$R_e = R_T - R_1 = 8.0 \times 10^3\ \Omega - 6.0 \times 10^3\ \Omega = 2.0 \times 10^3\ \Omega$$